

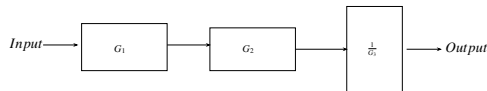
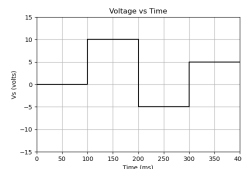


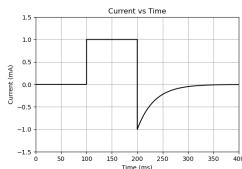
- 1) The pressure coil of a dynamometer type wattmeter is
 - a) highly inductive
 - b) highly resistive
 - c) purely resistive
 - d) purely inductive
- 2) The measurement system shown in the figure uses three sub-systems in cascade whose gains are specified as G_1 , G_2 , and $\frac{1}{G_3}$. The relative small errors associated with each respective subsystem G_1 , G_2 , and G_3 are ϵ_1 , ϵ_2 , and ϵ_3 . The error associated with the output is:



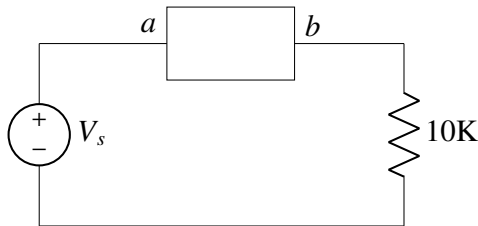
- a) $\epsilon_1 + \epsilon_2 + \frac{1}{\epsilon_3}$
 - b) $\frac{\epsilon_1 \cdot \epsilon_2}{\epsilon_3}$
 - c) $\epsilon_1 + \epsilon_2 - \epsilon_3$
 - d) $\epsilon_1 + \epsilon_2 + \epsilon_3$
- 3) The following circuit has a source voltage V_s as shown in the graph. The current through the circuit is also shown. The element connected between a and b could be:




- a) A B

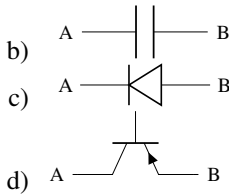

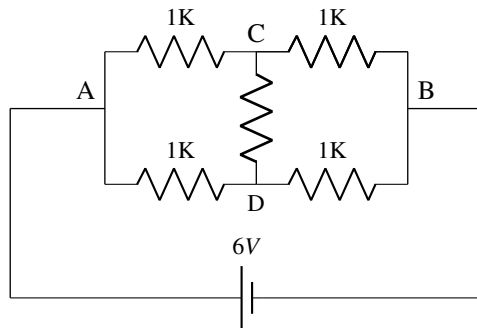- 4) The two inputs of a CRO are fed with two stationary periodic signals. In the X-Y mode, the screen shows a figure which changes from ellipse to circle and back to ellipse with its major axis changing orientation slowly and repeatedly. The following inference can be made from this:
- The signals are not sinusoidal
 - The amplitudes of the signals are very close but not equal
 - The signals are sinusoidal with their frequencies very close but not equal
 - There is a constant but small phase difference between the signals
- 5) The increasing order of speed of data access for the following devices is:
- Cache Memory
 - CDROM
 - Dynamic RAM
 - Processor Registers
 - Magnetic Tape
- (v), (ii), (iii), (iv), (i)
 - (v), (iii), (ii), (i), (iv)
 - (ii), (i), (iii), (iv), (v)
 - (v), (iv), (i), (iii), (ii)
- 6) A field excitation of 20 A in a certain alternator results in an armature current of 400 A in short circuit and a terminal voltage of 2000 V on open circuit. The magnitude of the internal voltage drop within the machine at a load current of 200 A is:
- 1 V
 - 10 V
 - 100 V
 - 1000 V
- 7) The current through the 2 k Ω resistance in the circuit shown is:
- 0 mA
 - 1 mA
 - 2 mA
 - 6 mA
- 8) Out of the following plant categories, the base load power plants are:
- Nuclear
 - Run-of-river
 - Pump Storage
 - Diesel



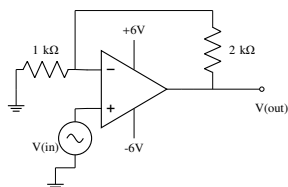- a) (i) and (ii)
 b) (ii) and (iii)
 c) (i), (ii) and (iv)
 d) (i), (iii) and (iv)
- 9) For a fixed value of complex power flow in a transmission line having a sending end voltage V , the real power loss will be proportional to:
- a) V
 b) V^2
 c) $\frac{1}{V^2}$
 d) $\frac{1}{V}$
- 10) How many 200W/220V incandescent lamps connected in series would consume the same total power as a single 100W/220V incandescent lamp?
- a) not possible
 b) 4
 c) 3
 d) 2
- 11) A Linear Time Invariant system with an impulse response $h(t)$ produces output $y(t)$ when input $x(t)$ is applied. When the input $x(t - \tau)$ is applied to a system with impulse response $h(t - \tau)$, the output will be
- a) $y(t)$
 b) $y(2(t - \tau))$
 c) $y(t - \tau)$
 d) $y(t - 2\tau)$
- 12) The nature of feedback in the opamp circuit shown is



- a) Current - Current feedback
- b) Voltage - Voltage feedback
- c) Current - Voltage feedback
- d) Voltage - Current feedback